
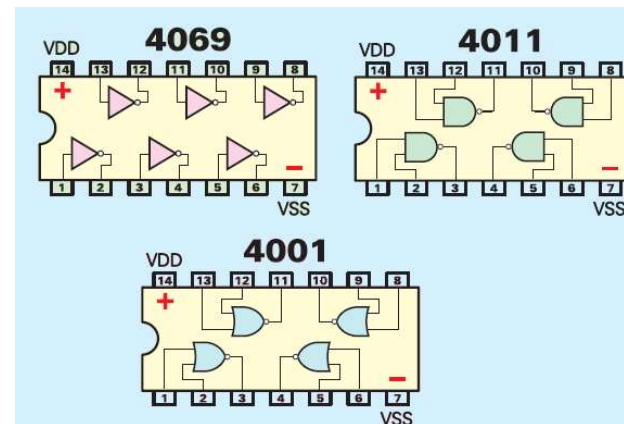


BOOLEAN LOGIC GATES

Chapter 10







INTRODUCTION

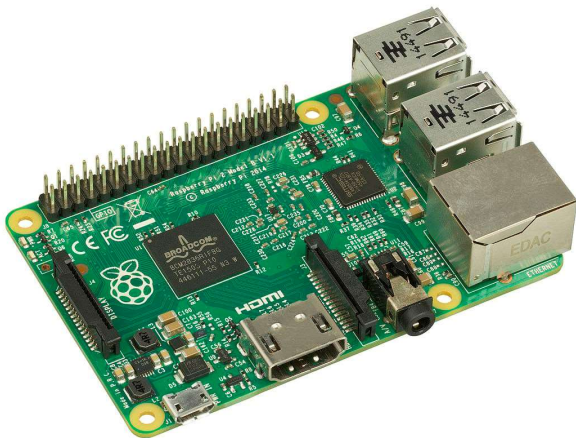- ❖ electronic circuits, memory devices and controlling devices are made of thousands of logic gates



INTRODUCTION

❖ types of logic gates

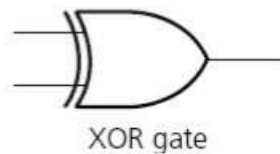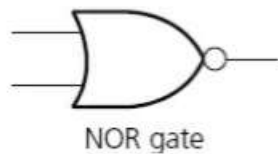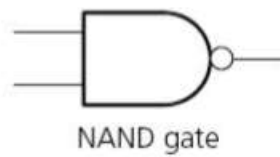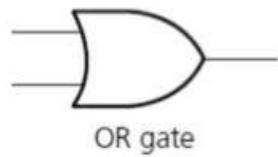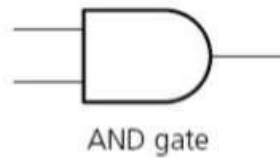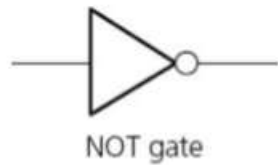

❖ truth table

❖ to trace the output from a logic circuit


Inputs	
A	B
0	0
0	1
1	0
1	1

Inputs		
A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	0
1	1	0
1	1	1

Inputs			
A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

NOT GATE

❖ example, NOT A

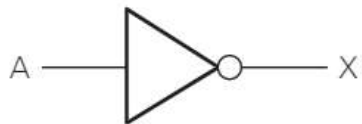

▲ Figure 10.2

Description:	Truth table:	How to write this:								
The output, X, is 1 if: the input, A, is 0	▼ Table 10.2 <table border="1"><thead><tr><th>Input</th><th>Output</th></tr><tr><th>A</th><th>X</th></tr></thead><tbody><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></tbody></table>	Input	Output	A	X	0	1	1	0	X = NOT A (logic notation) X = \bar{A} (Boolean algebra)
Input	Output									
A	X									
0	1									
1	0									

AND GATE

❖ example, A AND B



▲ Figure 10.3

Description:	Truth table:	How to write this:																		
The output, X, is 1 if: both inputs, A and B, are 1	▼ Table 10.3 <table border="1"><thead><tr><th colspan="2">Inputs</th><th>Outputs</th></tr><tr><th>A</th><th>B</th><th>X</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></tbody></table>	Inputs		Outputs	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1	X = A AND B (logic notation) X = A . B (Boolean algebra)
Inputs		Outputs																		
A	B	X																		
0	0	0																		
0	1	0																		
1	0	0																		
1	1	1																		

OR GATE

❖ example, A OR B



▲ Figure 10.4

Description:	Truth table:	How to write this:																		
The output, X, is 1 if: either input, A or B, or both, are 1	<p>▼ Table 10.4</p> <table border="1"><thead><tr><th colspan="2">Inputs</th><th>Output</th></tr><tr><th>A</th><th>B</th><th>X</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></tbody></table>	Inputs		Output	A	B	X	0	0	0	0	1	1	1	0	1	1	1	1	$X = A \text{ OR } B$ (logic notation) $X = A + B$ (Boolean algebra)
Inputs		Output																		
A	B	X																		
0	0	0																		
0	1	1																		
1	0	1																		
1	1	1																		

NAND GATE (NOT AND)

❖ example, A NAND B



▲ Figure 10.5

Description:	Truth table:	How to write this:																		
The output, X, is 1 if: input A AND input B are NOT both 1	▼ Table 10.5 <table border="1"><thead><tr><th colspan="2">Inputs</th><th>Output</th></tr><tr><th>A</th><th>B</th><th>X</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></tbody></table>	Inputs		Output	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0	$X = A \text{ NAND } B$ (logic notation) $X = \overline{A \cdot B}$ (Boolean algebra)
Inputs		Output																		
A	B	X																		
0	0	1																		
0	1	1																		
1	0	1																		
1	1	0																		

NOR GATE (NOT OR)

❖ example, A NOT OR B



▲ Figure 10.6

Description:	Truth table:	How to write this:																		
The output, X, is 1 if: neither input A nor input B is 1	▼ Table 10.6 <table border="1"><thead><tr><th colspan="2">Inputs</th><th>Output</th></tr><tr><th>A</th><th>B</th><th>X</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></tbody></table>	Inputs		Output	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0	X = A NOR B (logic notation) X = $\overline{A + B}$ (Boolean algebra)
Inputs		Output																		
A	B	X																		
0	0	1																		
0	1	0																		
1	0	0																		
1	1	0																		

XOR GATE (EXCLUSIVE OR)

❖ example, A XOR B




▲ Figure 10.7

Description:	Truth table:	How to write this:																		
<p>The output, X, is 1 if: (input A is 1 AND input B is 0) or (input A is 0 AND input B is 1)</p>	<p>▼ Table 10.7</p> <table border="1"><thead><tr><th colspan="2">Inputs</th><th>Output</th></tr><tr><th>A</th><th>B</th><th>X</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></tbody></table>	Inputs		Output	A	B	X	0	0	0	0	1	1	1	0	1	1	1	0	<p>$X = A \text{ XOR } B$ (logic notation)</p> <p>$X = (A \cdot \bar{B}) + (\bar{A} \cdot B)$ (Boolean algebra)</p> <p>NOTE: this is sometimes written as: $(A + B) \cdot (\bar{A} \cdot \bar{B})$</p>
Inputs		Output																		
A	B	X																		
0	0	0																		
0	1	1																		
1	0	1																		
1	1	0																		


LOGIC CIRCUIT (TYPE I)

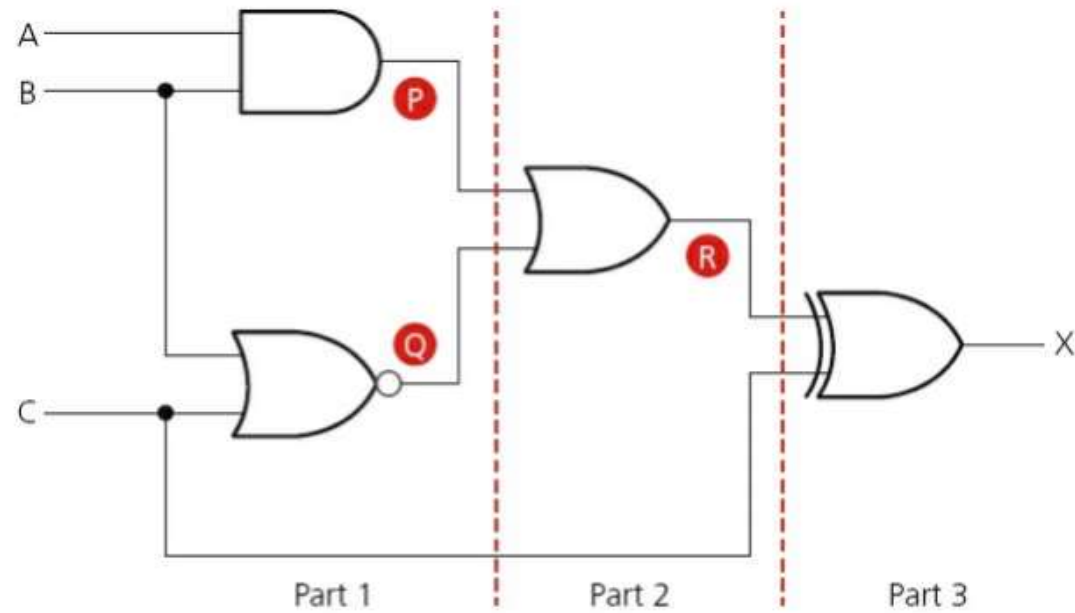❖ Produce truth table from this logic circuit



LOGIC CIRCUIT (TYPE I)


❖ Part one

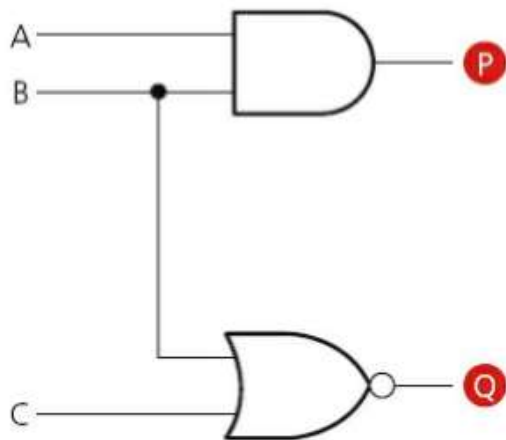

Input values			Output values	
A	B	C	P	Q
0	0	0	0	1
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	1
1	0	1	0	0
1	1	0	1	0
1	1	1	1	0

LOGIC CIRCUIT (TYPE I)


❖ Part two

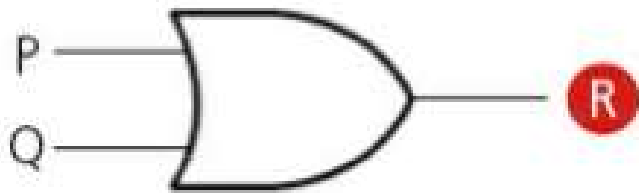

Input		Output
P	Q	R
0	1	1
0	0	0
0	0	0
0	0	0
0	1	1
0	0	0
1	0	1
1	0	1

LOGIC CIRCUIT (TYPE I)

❖ Part three

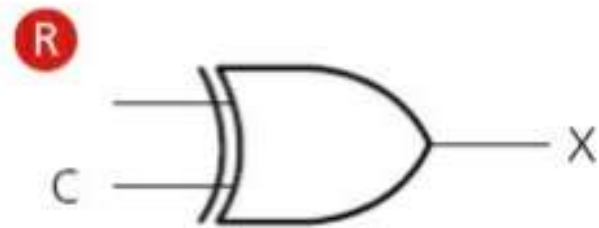

Inputs		Output
R	C	X
1	0	1
0	1	1
0	0	0
0	1	1
1	0	1
0	1	1
1	0	1
1	1	0


LOGIC CIRCUIT (TYPE I)

❖ Truth table


Input values			Intermediate values			Output
A	B	C	P	Q	R	X
0	0	0	0	1	1	1
0	0	1	0	0	0	1
0	1	0	0	0	0	0
0	1	1	0	0	0	1
1	0	0	0	1	1	1
1	0	1	0	0	0	1
1	1	0	1	0	1	1
1	1	1	1	0	1	0

Input values			Output
A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


LOGIC CIRCUIT (TYPE I) EXERCISE

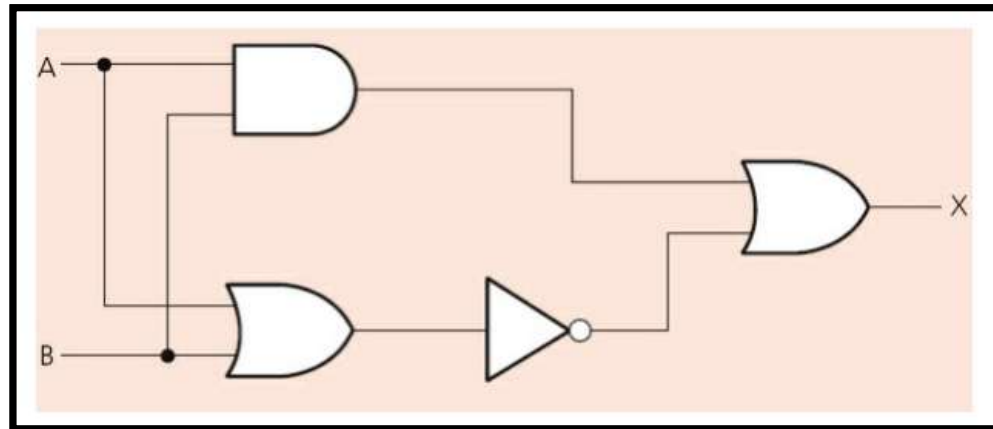

LOGIC CIRCUIT (TYPE I) EXERCISE

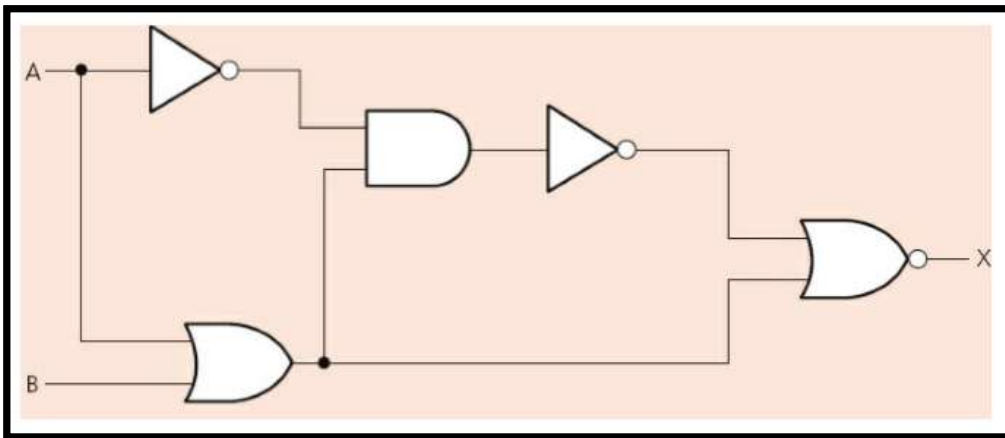

LOGIC CIRCUIT (TYPE I) EXERCISE

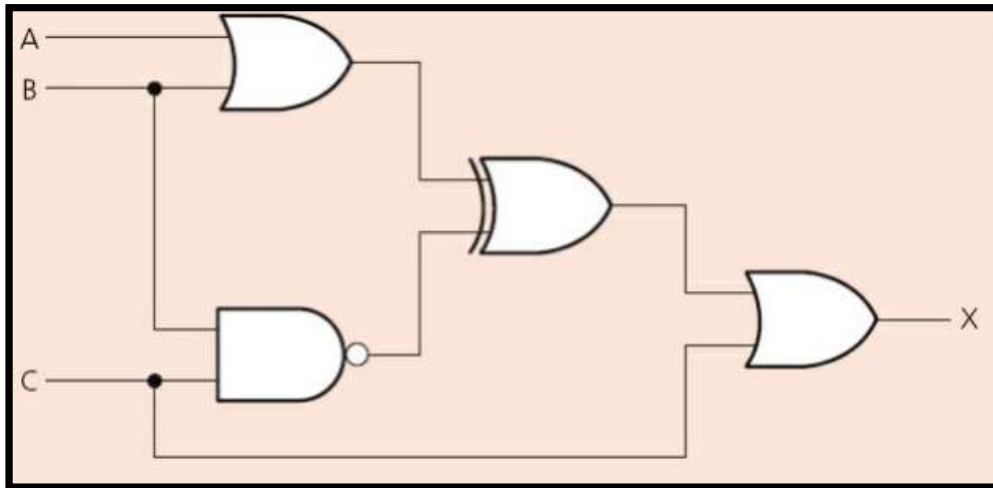

LOGIC CIRCUIT (TYPE I) EXERCISE

